

SOLUTIONSProblem 1:Given PV Cell Parameters

Cell area : 0.005 m^2

Reverse saturation Current $I_0 = 10^{-11}$ Amps

Insolation : 1000 W/m^2

Short-Circuit Current $I_{sc} : \text{~~1.5~~ 1.5}$ Amps

Temperature : 25°C

a) Cell Open Circuit Voltage :

$$V_{oc} = 0.0257 \ln \left(\frac{I_{sc}}{I_0} + 1 \right) \text{ Volts}$$

$$= 0.0257 \ln \left(\frac{1.5}{10^{-11}} + 1 \right) \text{ Volts}$$

$$\approx 0.0257 \ln \left(\frac{1.5}{10^{-11}} \right)$$

$$= 0.0257 \times 24.73 = \underline{0.6613 \text{ Volts.}}$$

b) The load Current when the O/P Voltage is 0.5 Volts

$$\text{Diode Current } I_d = I_0 \left(e^{\frac{qV_d}{KT}} - 1 \right)$$

$$q = 1.602 \times 10^{-19} \text{ Coulombs, } K = 1.381 \times 10^{-23} \text{ Boltzmann's Const.}$$

$$T = \text{Temp. in Kelvin} = 273 + 25 = 298 \text{ K}$$

$$\text{Then } I_d = I_0 \left[e^{38.9 V_d} - 1 \right]$$


$V_d \rightarrow$ Diode Volt. drop.

$$I_d = 10^{-11} \left[e^{38.9 \times 0.6} - 1 \right]$$

$$= 10^{-11} \left[e^{23.34} - 1 \right] = 0.137 \text{ Amps}$$

$$= \underline{137 \text{ mA}}$$

$$\text{Now } I = I_{sc} - I_d$$

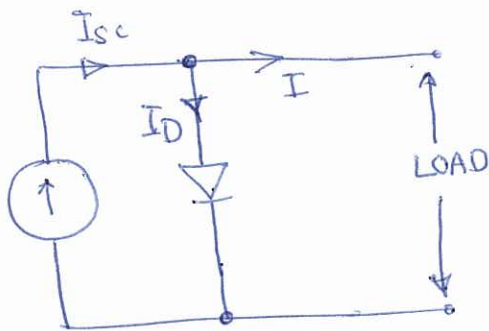

PV Equivalent Circuit

$$\text{Accordingly } I = 1.5 - 0.137 = 1.363 \text{ Amps}$$

c) Power delivered to the load = $1.36 \times 0.5 = 0.68 \text{ Watts}$

d) Efficiency of the cell at $V = 0.5 \text{ Volts}$.

$$\eta \% = \frac{P_{out}}{P_{in}} \times 100$$

$$P_{out} = 0.68 \text{ Watts} ; \quad P_{in} = 1000 \text{ W/m}^2 \times 0.005 \text{ m}^2 \text{ area}$$

$$= 5 \text{ Watts Solar Power I/P}$$

$$\therefore \eta \% = \frac{0.68}{5} \times 100 = \underline{13.6 \%}$$

Problem 2 :

$$T_{\text{cell}} = T_{\text{ambient}} + \left(\frac{\text{NOCT} - 20}{0.8} \right) \cdot S \quad \leftarrow \text{in kW/m}^2$$

$$\begin{aligned} \text{a) } T_{\text{cell}} &= 25 + \left(\frac{50 - 20}{0.8} \right) \cdot 1 \\ &= 25 + 37.5 = 62.5^\circ\text{C} \end{aligned}$$

Max. Power drops by 0.5 % / deg C

PV module Power = 100 Watts (Given)

So, Max. Power @ ambient temp. of 25°C is

$$\begin{aligned} P_{\text{max}} &= 100 \left[1 - 0.005 (62.5 - 25) \right] \\ &= 100 \left[1 - 0.005 (37.5) \right] \\ &= 81.75 \text{ Watts} \end{aligned}$$

∴ Drop of 18.75 % from the module power of 100 Watt.

$$\begin{aligned} \text{b) } T_{\text{cell}} &= 0 + \left(\frac{45 - 20}{0.8} \right) \times 0.5 \\ &= \left(\frac{25}{0.8} \right) \times 0.5 = 15.625^\circ\text{C} \end{aligned}$$

$$\begin{aligned} P_{\text{max}} &= 100 \left[1 - 0.005 (15.625 - 0) \right] \\ &= 92.1875 \text{ Watts} \end{aligned}$$

∴ Drop of 7.81 % from the rated power of 100 Watts.

$$c) T_{cell} = 30 + \left(\frac{45-20}{0.8} \right) \times 0.8$$

$$= 30 + 25 = 55^{\circ}C$$

$$P_{max} = 100 \left[1 - 0.005 (55 - 30) \right]$$


$$= 87.5 \text{ Watts}$$

\therefore Drop of 12.5% from the rated power of 100 Watts.

3) 40 Cells in series $\rightarrow 40 \times 0.5V = 20 \text{ Volts}$.

if 1 Cell is shorted, there will be 39 Cells - good ones

$$39 \times 0.5V = 19.5 \text{ Volts}$$

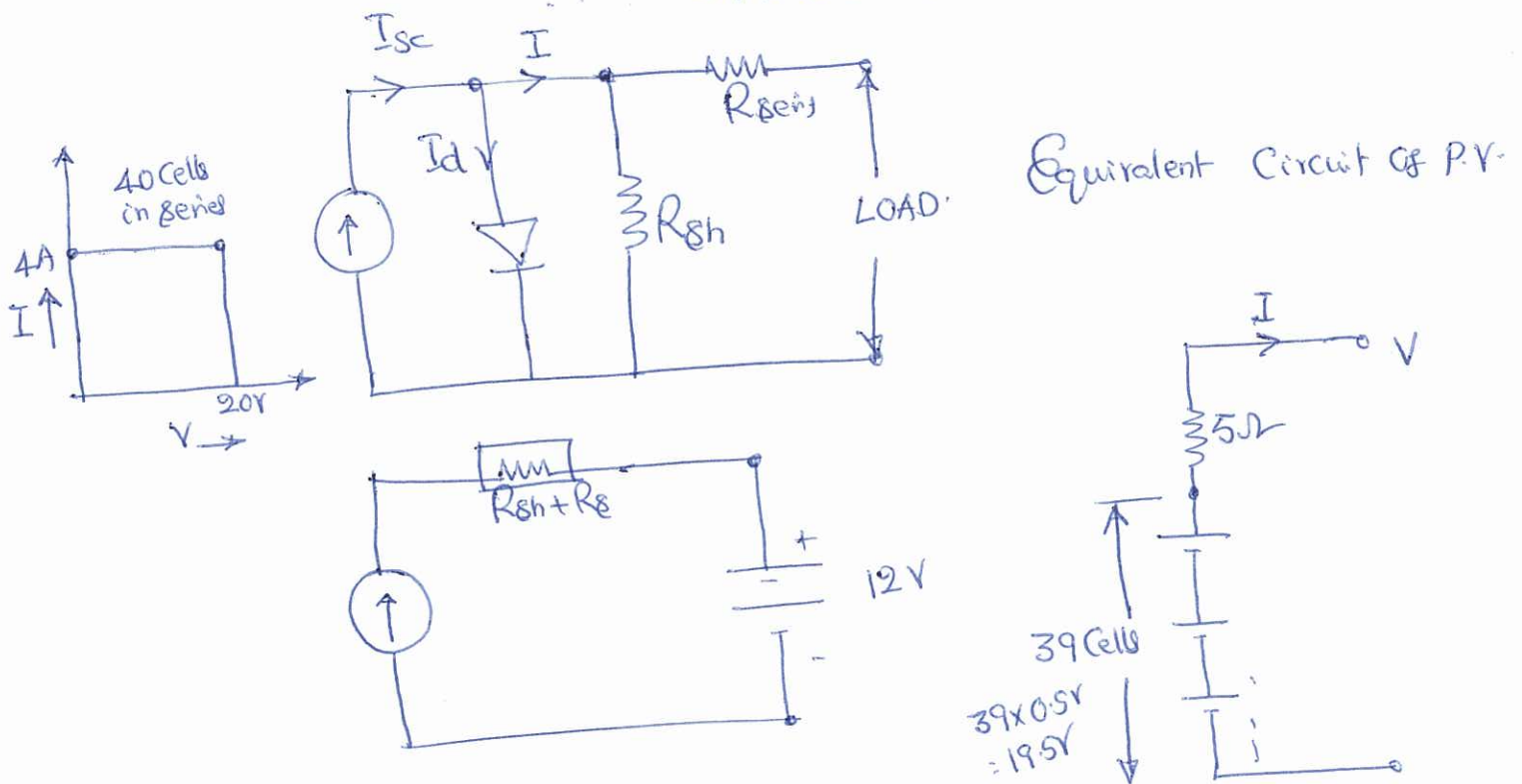

$$I_{Battery} = \frac{19.5V - 12V}{5\Omega}$$

$$= 1.5 \text{ Amps}$$

\therefore Current is 1.5 Amps instead of 4 Amps.